

HOMEWORK I (Part I)

Due day: 9:00am Oct.11 (Thursday), 2012

This homework is to let you familiar with tools and Verilog language. It includes A) basic exercises and B) the first part of a simplified multi-cycle (**SMILE**) CPU with only 17 instructions shown in the last page. Part B is to let the first-time CPU designer be familiar with the instruction set architecture, dataflow modeling and controller design. Some problems have reference code. They are for your reference only. Most likely, you need to modify them to fit the problem specification.

General rules for deliverables

- This homework needs to be completed by INDIVIDUAL student.
- Compress all files described in the problem statements into one zip or rar.
- Submit the compress file to the course website before the due day. **Warning!**
AVOID submit in the last minute. Late submission is not accepted.

Grading Notes

- **Important!** DO remember to include your Verilog code. NO code, NO grades. Also, if your code can not be recompiled by TA successfully using tools in SoC Lab, you receive NO credit.
- Write your report seriously and professionally. Incomplete description and information will reduce your chances to get more credits.
- If extra works (like synthesis, post-simulation or additional instructions) are done, please describe them in your final report clearly for bonus points.
- Please follow course policy.

Deliverables

1. All CPU Verilog codes including components, testbenches and machine code for each lab exercise. NOTE: Please DO NOT include source code in the report!
2. A homework report that includes
 - a. A summary in the beginning to state what has been done (such as SMILE CPU, synthesis, post-synthesis simulation, additional branch instruction with verification);
 - b. Simulated waveforms with proper explanation;
 - c. Report requirements in each assignment;

HOMEWORK I (Part I)

- d. Learned lessons (skills learned, where do you stuck most and what do you find, exciting things etc.)
3. Please write in MS word using the Homework report template and **follow the convention for the file name** of your report: **n26984795_ 李 大 鳴 _hw1p1_report.doc**

1. (10/100) Write and verify Verilog a 16-bit performance counter by using two universal 8-bit counter/timer with the following specification:

Universal 8-bit counter/timer Design Requirements

- a. Number format: unsigned
- b. Inputs: *clk* (1 bit), *_areset* (1 bit), *_aset* (1 bit), *_load* (1 bit), *preld-val* (8 bit), *_updown* (1 bit), *_wrapstop* (1 bit)
- c. Outputs: *dcout*(8 bit), *overflow*(1 bit),
- d. The counter is triggered by the clock signal (*clk*).
- e. *_areset* =1 makes the counter set to zero asynchronously, while *_aset* =1 let the counter set to its maximum value asynchronously. If none of them are high, the counter is operated regularly.
- f. If the signal *load* is active (high), the the preload value (*preld-val*) will be loaded, otherwise, no effect to the counter.
- g. The priority of the control signal is *_areset* > *_aset* > *_load*. This is to avoid un-intentionally activate these three signals at the same time.
- h. *_updown* indicates whether the counter is counted upward (when high) or downward (when low).
- i. *_wrapstop* is used to set the counting behavior. If *_wrapstop* = 1, the counter will wrap around. (Ex. If the counting is upward , the counter will go back to zero and then recount again.) If *_wrapstop* = 0, the counter will stop and issue *overflow*.
- j. If the result is out of range, *overflow* will be flagged to logic 1, otherwise, 0.
- k. You may add other signal additional pins and function as long as you clearly specify and explain.
- l. Hierarchy design is allowed; however, they must be specified.
- m. The design shall be implemented by using structural style and be able to identified major components.

Report Requirements

- a. Proper explanation of your design is required for full credits.

HOMEWORK I (Part I)

- b. A figure (block diagram with logic gates) shall be draw to depict your design in the end.
- c. Verify your code with a testbench. This testbench needs to show all major situations. Show your snapshot of waveform for different cases in your reports and illustrate the correctness of your results.
- d. Synthesize this counter and re-run testbenches on the synthesized code and observe your waveforms. Provide a snapshot of the waveform and pin point the location of dubious errors. the synthesized block diagram, gates that are actually used by the synthesizer and report 5 most frequent warning/errors during synthesis.
- e. Use nLint to analyze your code, report the final results and 3~5 most frequent warning/errors in your code.

HOMEWORK I (Part I)

2. (20/100) Write and verify a 32-bit ALU that could perform the following arithmetic and logic operations:

- **Logic operations: AND, OR, XOR, NOP**
- **Arithmetic operations: ADD, SUB**
- **Shift & Rotate operations: SLLI (Shift Left Immediate), SRLI (Shift Right Immediate) and ROTRI (Rotate Right Immediate)**
- **Instruction set architecture could be found on Page 8-9.**

The ALU unit shown in Fig. 2 has two data inputs (SCR1 and SCR2) and one data output (ALU_result) along with one output flag, ALU_Overflow. Controlling signals are *opcode*, *sub_opcode* and *Enable_execute*. *opcode* and *sub_opcode* will be used to select which operation to be executed

 


Fig. 2 Conceptual Diagram of the ALU

This ALU consists of three different combinational circuit building blocks:

- Add/Sub to perform addition and subtraction arithmetic operations
- Logic block to perform logical operations
- Barrel Shifter to perform shift and rotate operations

Design Requirements

- This ALU shall be designed such that it could be compatible with the given ISA and instruction format.
- The ALU will be used in subsequent Homework 1-Part 2. So you shall be aware that more instructions and mechanisms will be added later. When design, please give room for extension.
- A skeleton code is given for quick startup. However, it still needs to be modified to fully work.
- The ALU needs to be verified with proper testbenches for each instruction.

HOMEWORK I (Part I)

Report Requirements

- Proper explanation of your design is required for full credits.
- A figure (block diagram with logic gates) shall be drawn to depict your design in the end.
- Verify your code with a testbench before synthesis. This testbench needs to show all major situations. Show your snapshot of waveform for different cases in your reports and illustrate the correctness of your results.
- Synthesize this ALU and re-run testbenches on the synthesized code and observe your waveforms. Provide a snapshot of the waveform and pin point the location of dubious errors, the synthesized block diagram, gates that are actually used by the synthesizer and report 5 most frequent warning/errors during synthesis.
- Use nLint to analyze your code, report the final results and 3~5 most frequent warning/errors in your code.

Its major portion of the Verilog may look like as follows.

```
Add/Sub block (add sub module in reference code1 for ALU):
assign result=(control == 0)?(operand2+operand1):(operand2-operand1);

Logic block
and_result=src2&src1;
or_result=src2|src1;
xor_result=src2^src1;

Shift block (Barrel Shifter module in reference code1 for ALU):
output [31:0] result; // result operand
reg [95:0] rotate_reg;
input [31:0] in1,in2;// input operand; in1: # of shifts; in2: original data
rotate_reg={in2,in2,in2};

✦ Rotate Operation:
rotate_reg=(direction)?rotate_reg>>in1:rotate_reg<<in1;
result=rotate_reg[63:32];

✦ Shift Operation:
result=(direction)?in2>>in1:in2<<in1;
```

HOMEWORK I (Part I)

Reference code for ALU

```
module alu(alu_result,alu_overflow,scr1,scr2,opcode,sub_opcode,enable_execute,reset);
    parameter NOP=5'b01001,ADD=5'b00000,SUB=5'b00001,AND=5'b00010,
              OR=5'b00100,XOR=5'b00011,SRLI=5'b01001,SLLI=5'b01000,
              ROTRI=5'b01011;
    output reg [31:0]alu_result;
    output reg alu_overflow;

    input [31:0]scr1,scr2;
    input [5:0]opcode;
    input [4:0]sub_opcode;
    input reset;
    input enable_execute;

    reg [63:0]rotate;
    reg a,b;

    always @ ( * )begin
        if(reset)begin
            alu_result=32'b0;
            alu_overflow=1'b0;
        end
        else if(enable_execute)begin
            case(opcode)
                6'b100000 : case (sub_opcode)
                    NOP : begin
                        alu_result=32'b0;
                        alu_overflow=1'b0;
                    end
                    ADD : begin
                        {a,alu_result[30:0]}=scr1[30:0]+scr2[30:0];
                        {b,alu_result[31]}=scr1[31]+scr2[31]+a;
                        alu_overflow=a ^ b;
                    end
                    SUB : begin
                        {a,alu_result[30:0]}=scr1[30:0]-scr2[30:0];
                        {b,alu_result[31]}=scr1[31]-scr2[31]-a;
                        alu_overflow=a ^ b;
                    end
                endcase
            endcase
        end
    end
```

HOMEWORK I (Part I)

```
AND    : begin
        alu_overflow=1'b0;
        alu_result=scr1&scr2;
    end
OR      : begin
        alu_overflow=1'b0;
        alu_result=scr1|scr2;
    end
XOR     : begin
        alu_overflow=1'b0;
        alu_result=scr1^scr2;
    end
SRLI    : begin
        alu_overflow=1'b0;
        alu_result=scr1>>scr2;
    end
SLLI    : begin
        alu_overflow=1'b0;
        alu_result=scr1<<scr2;
    end
ROTRI   : begin
        alu_overflow=1'b0;
        rotate={scr1,scr1}>>scr2;
        alu_result=rotate[31:0];
    end
default : begin
        alu_overflow=1'b0;
        alu_result=32'b0;
    end
endcase

6'b101000 : begin
    {a,alu_result[30:0]}=scr1[30:0]+scr2[30:0];
    {b,alu_result[31]}=scr1[31]+scr2[31]+a;
    alu_overflow=a ^ b;
end
6'b101100 : begin
    alu_overflow=1'b0;
    alu_result=scr1|scr2;
end
6'b101011 : begin
    alu_overflow=1'b0;
    alu_result=scr1^scr2;
end
default : begin
    alu_overflow=1'b0;
    alu_result=32'b0;
end
endcase
end
else begin
    alu_result=32'b0;
    alu_overflow=1'b0;
end
end
endmodule
```

HOMEWORK I (Part I)


SMILE Processor Instruction Set Architecture (ISA)

We will follow ISA in this homework and for the rest of homeworks. Please read the ISA carefully. Your design needs to comply with this ISA. It is NOTED that you SHALL NOT revise by yourself. If you have any questions, please talk to TA first.


BASICS

☞ Data-processing (SE:sign-extended, ZE:zero-extended)

 
*** Note that NOP and SRLI has the same OP + sub OP. This is durable. If you examine their DST, SRC1 and SRC2, you will be able to find their differences and find a proper way to implement.



OP code	Mnemonics	DST	SRC1	SRC2	Sub OP	Description
100000	NOP	00000	00000	00000	01001	No operation
100000	ADD	\$Rt	\$Ra	\$Rb	00000	$Rt = Ra + Rb$
100000	SUB	\$Rt	\$Ra	\$Rb	00001	$Rt = Ra - Rb$
100000	AND	\$Rt	\$Ra	\$Rb	00010	$Rt = Ra \& Rb$
100000	OR	\$Rt	\$Ra	\$Rb	00100	$Rt = Ra Rb$
100000	XOR	\$Rt	\$Ra	\$Rb	00011	$Rt = Ra \wedge Rb$
100000	SRLI	\$Rt	\$Ra	imm	01001	Shift right : $Rt = Ra \gg imm$
100000	SLLI	\$Rt	\$Ra	imm	01000	Shift left : $Rt = Ra \ll imm$
100000	ROTRI	\$Rt	\$Ra	imm	01011	Rotate right : $Rt = Ra \gg imm$

 

OP code	Mnemonics	DST	SRC1	SRC2	Description
101000	ADDI	\$Rt	\$Ra	imm	$Rt = Ra + SE(imm)$
101100	ORI	\$Rt	\$Ra	imm	$Rt = Ra ZE(imm)$
101011	XORI	\$Rt	\$Ra	imm	$Rt = Ra \wedge ZE(imm)$

 

HOMEWORK I (Part I)

OP code	Mnemonics	DST	SRC1	Description
100010	MOVI	\$Rt	imm	Rt = SE(immmediate)

//////////////////////////////////// Reference //////////////////////////////////////

☞ SMILE CPU has the following instruction format (**Andes ISA compatible**)

The Andes 32bit instruction formats and the meaning of each filed are described below:

➤ Type-0 Instruction Format

0	Opc_6	{sub_1, imm_24}			
---	-------	-----------------	--	--	--

➤ Type-1 Instruction Format

0	Opc_6	rt_5	imm_20		
0	Opc_6	rt_5	sub_4	imm_16	

➤ Type-2 Instruction Format

0	Opc_6	rt_5	ra_5	imm_15	
0	Opc_6	rt_5	ra_5	{sub_1, imm_14}	

➤ Type-3 Instruction Format

0	Opc_6	rt_5	ra_5	rb_5	sub_10
0	Opc_6	rt_5	ra_5	imm_5	sub_10

➤ Type-4 Instruction Format

0	Opc_6	rt_5	ra_5	rb_5	rd_5	sub_5
0	Opc_6	rt_5	ra_5	imm1_5	imm2_5	sub_5

- ◆ opc_6: 6-bit opcode
- ◆ rt_5: target register in 5-bit index register set
- ◆ ra_5: source register in 5-bit index register set
- ◆ rb_5: source register in 5-bit index register set
- ◆ rd_5: destination register in 5-bit index register set
- ◆ sub_10: 10-bit sub-opcode
- ◆ sub_5: 5-bit sub-opcode
- ◆ sub_4: 4-bit sub-opcode
- ◆ sub_1: 1-bit sub-opcode
- ◆ imm_24: 24-bit immediate value, for unconditional jump instructions (J, JAL). The immediate value is used as the lower 24-bit offset of same 32MB memory block (new
- ◆ PC[31:0] = {current PC[31:25], imm_24, 1'b0}
- ◆ imm_20: 20-bit immediate value. Sign-extended to 32-bit for MOVI operations.
- ◆ imm_16: signed PC relative address displacement for branch instructions.
- ◆ imm_15: 15-bit immediate value. Zero extended to 32-bit for unsigned operations, while sign extended to 32-bit for signed operations.
- ◆ imm_14: signed PC relative address displacement for branch instructions.
- ◆ imm_5, imm1_5, imm2_5: 5-bit unsigned count value or index value

////////////////////////////////////